

Final Exam
AB E 312 Electrical Power
December 07, 2002

Calculators allowed. No other aids permitted.
Answer all questions on the exam sheets.

Maximum 3 hours

- (10) 1) Define the following terms. Use sketches, equations and circuit diagrams as necessary. You must describe what each term is or means. Simply indicating how a term may be calculated, as an example, will not be sufficient to receive full marks.
- a) over compound generator
 - b) armature reaction
 - c) synchronous motor
 - d) locked rotor
 - e) transformer

- (2) 2) How do manufacturers design induction motors so that they can be connected to run at either of two distinct voltages?
- (2) 3) Why is it necessary to have overcurrent protection in addition to the 15-A circuit breaker for an induction motor rated at $\frac{3}{4}$ HP, 230 V, 5.5 A, 60 Hz, 1 phase, 1725 RPM?
- (2) 4) List two benefits of having an inverter (variable frequency drive) controlling a three phase induction motor?
- (2) 6) How would you reverse the direction of rotation for a single phase capacitor-start induction-run motor?
- (2) 7) How many switches and of what type would be required to control an incandescent safety light from four locations?
- (2) 8) Compare and contrast the level of protection offered by a thermal breaker and a thermal breaker with a ground-fault circuit interrupter.
- (2) 9) A three phase induction motor on a conveyor belt is rated at 25 HP, 460 V, 34 A, 1740 RPM, Power Factor of 0.95, and Efficiency of 90%. In a routine check of the motor you measure a source voltage of 455 V and a source current of 28 A. Verbally describe how the other ratings (speed, output power, power factor and efficiency) may be different.

- (3) 10) Your Christmas light display causes a 15-A SPST breaker to trip. Your roommate suggests replacing it with a 30 A SPST breaker. Explain your response.
- (3) 11) How does the magnetic starter coil in the lab rated for 115 VAC provide low voltage protection to the motor?
- (10) 12) Each pole of a 100-kW, 250-V flat compound DC generator has a shunt field of 1900 turns and a series field of 10 turns. If the total shunt-field resistance, the armature resistance and series field resistance is $100\ \Omega$, $0.2\ \Omega$ and $0.1\ \Omega$, respectively, what is the voltage generated at the armature under full load conditions?

- (4) 13) An inverter is used to supply electrical energy to a 4-pole single-phase motor at a frequency of 43 Hz. If the rotor slip is 4%, what is the rotational speed of the shaft?
- 14) A 3-phase heater dissipates 15 kW when connected to a 208-V, 3-phase line.
- (2) a) What is the line current if the resistors are connected in wye?
 - (2) b) What is the line current if the resistors are connected in delta?
 - (2) c) If the resistors are known to be connected in wye, what is the resistance of each?

15) The effective impedances of the main and auxiliary windings of a split-phase motor under locked rotor conditions are:

	Effective Resistance (Ω)	Effective Reactance (Ω)
Main winding	5	10
Auxiliary winding	8	6

If the line voltage is 123 V, calculate

- (3)
- (2)
- (5)
- (5)
- a) the magnitude of the currents in the auxiliary and main windings,
- b) the phase angle between the current in the auxiliary winding and the current in the main winding,
- c) the line current and
- d) the power factor under locked-rotor conditions.

The End

** Merry Christmas **

*****This page intentionally left blank*****

*****This page intentionally left blank*****

*****This page intentionally left blank*****